

# SEQUENTIAL CIRCUITS

Mahdi Nazm Bojnordi

Assistant Professor

School of Computing

University of Utah


# Overview

---

- This lecture
  - ▣ Carry look-ahead Adder
  - ▣ Clock and sequential circuits
 
# Recall: Carry Ripple Adder

- Simplest design by cascading 1-bit boxes
  - ▣ Each 1-bit box sequentially implements AND and OR
  - ▣ Critical path: the total delay is the time to go through 64 gates
- How to make a 32-bit addition faster?



# Recall: Carry Ripple Adder

- Simplest design by cascading 1-bit boxes
  - ▣ Each 1-bit box sequentially implements AND and OR
  - ▣ Critical path: the total delay is the time to go through 64 gates
- How to make a 32-bit addition faster?
- **Recall:** any logic equation can be expressed as the sum of products (only 2 gate levels!)
  - ▣ Challenges: many parallel gates with very large inputs
  - ▣ **Solution:** we'll find a compromise

# Fast Adder

- Computing carry-outs
  - ▣  $\text{Carry}_{ln1} = b_0 \cdot \text{Carry}_{ln0} + a_0 \cdot \text{Carry}_{ln0} + a_0 \cdot b_0$
  - ▣  $\text{Carry}_{ln2} = b_1 \cdot \text{Carry}_{ln1} + a_1 \cdot \text{Carry}_{ln1} + a_1 \cdot b_1$
  - ▣  $\quad = b_1 \cdot b_0 \cdot c_0 + b_1 \cdot a_0 \cdot c_0 + b_1 \cdot a_0 \cdot b_0 +$
  - ▣  $\quad a_1 \cdot b_0 \cdot c_0 + a_1 \cdot a_0 \cdot c_0 + a_1 \cdot a_0 \cdot b_0 + a_1 \cdot b_1$
  - ▣ ...
  - ▣  $\text{Carry}_{ln32} =$  a really large sum of really large products
- Each gate is enormous and slow!

# Fast Adder

- Computing carry-outs: equation re-phrased
- $C_{i+1} = a_i \cdot b_i + a_i \cdot C_i + b_i \cdot C_i$
- $= (a_i \cdot b_i) + (a_i + b_i) \cdot C_i$
  
- Generate signal  $= a_i \cdot b_i$ 
  - The current pair of bits will generate a carry if they are both 1
- Propagate signal  $= a_i + b_i$ 
  - The current pair of bits will propagate a carry if either is 1
  
- Therefore,  $C_{i+1} = G_i + P_i \cdot C_i$

# Fast Adder

## □ Computing carry-outs: example

$$c_1 = g_0 + p_0.c_0$$

$$c_2 = g_1 + p_1.c_1 = g_1 + p_1.g_0 + p_1.p_0.c_0$$

$$c_3 = g_2 + p_2.g_1 + p_2.p_1.g_0 + p_2.p_1.p_0.c_0$$

$$c_4 = g_3 + p_3.g_2 + p_3.p_2.g_1 + p_3.p_2.p_1.g_0 + p_3.p_2.p_1.p_0.c_0$$

(1)

(2)

(3)

(4)

(4)

Either,

(1) a carry was just generated, or

(2) a carry was generated in the last step and was propagated, or

(3) a carry was generated two steps back and was propagated by both the next two stages, or

(4) a carry was generated N steps back and was propagated by every single one of the N next stages


# Fast Adder

- Divide and Conquer

- **Challenge:** for the 32<sup>nd</sup> bit, we must AND every single propagate bit to determine what becomes of c0 (among other things)

- **Solution:** the bits are broken into groups (of 4) and each group computes its group-generate and group-propagate

 - For example, to add 32 numbers, you can partition the task as a tree





# Fast Adder

- P and G for 4-bit blocks
  - Compute P0 and G0 (super-propagate and super-generate) for the first group of 4 bits (and similarly for other groups of 4 bits)
    - $P0 = p0.p1.p2.p3$
    - $G0 = g3 + g2.p3 + g1.p2.p3 + g0.p1.p2.p3$
  - Carry out of the first group of 4 bits is
    - $C1 = G0 + P0.c0$
    - $C2 = G1 + P1.G0 + P1.P0.c0$
    - $C3 = G2 + (P2.G1) + (P2.P1.G0) + (P2.P1.P0.c0)$
    - $C4 = G3 + (P3.G2) + (P3.P2.G1) + (P3.P2.P1.G0) + (P3.P2.P1.P0.c0)$
- By having a tree of sub-computations, each AND, OR gate has few inputs and logic signals have to travel through a modest set of gates (equal to the height of the tree)

# Fast Adder

## □ Example


Add	A	0001	1010	0011	0011
	B	1110	0101	1110	1011
	g	0000	0000	0010	0011
	p	1111	1111	1111	1011

P	1	1	1	0
G	0	0	1	0

C4 = 1

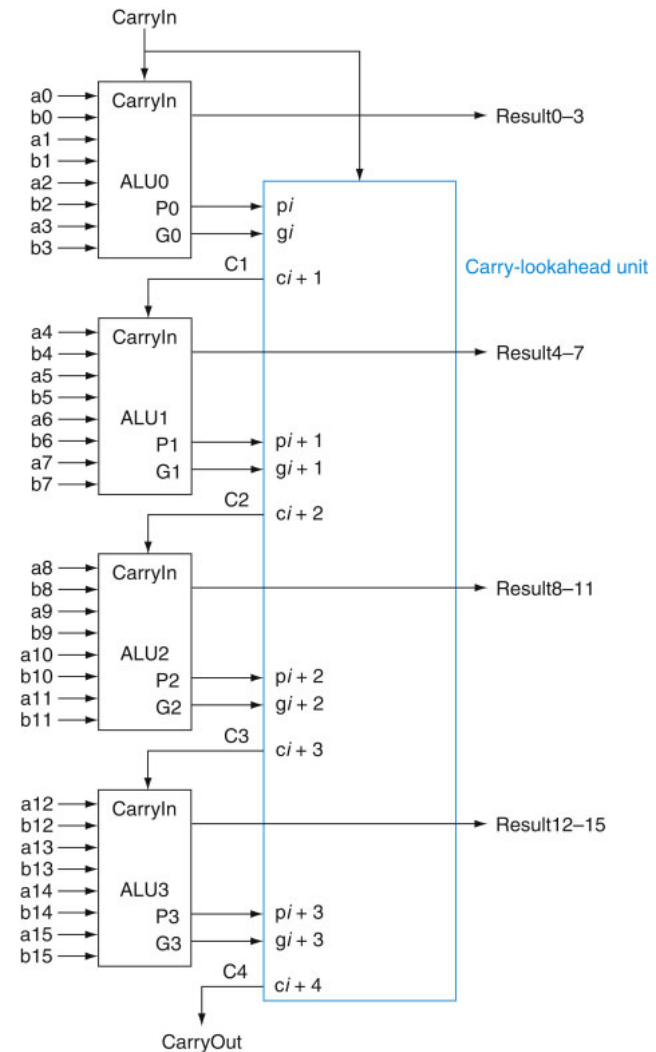
# Fast Adder: Carry Look-Ahead

- 16-bit Ripple-carry takes 32 steps
- This design takes how many steps?


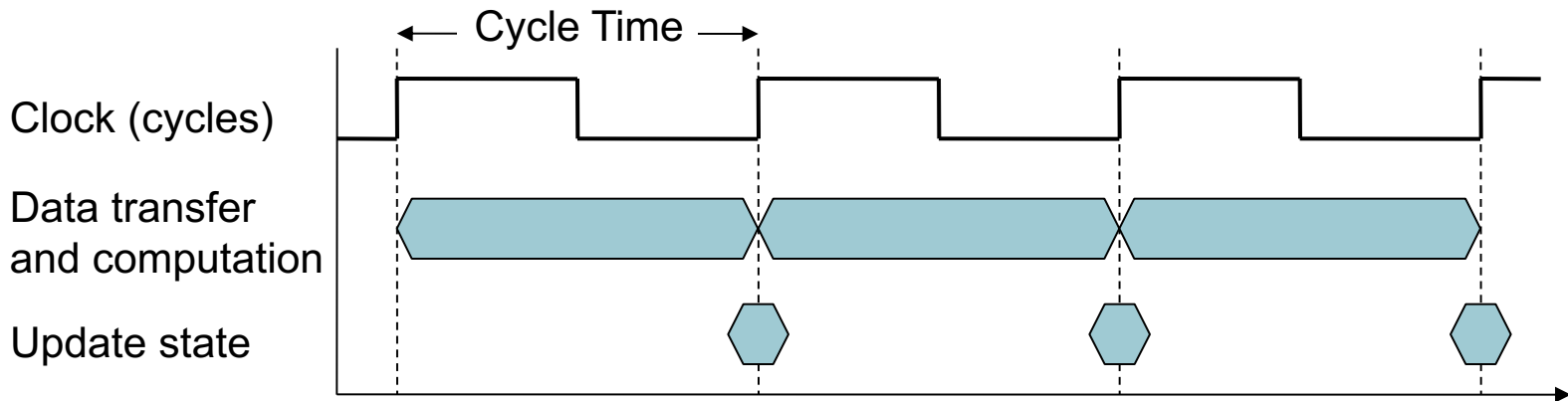
# Recall: Clocking and Cycle Time


- Operation of digital hardware governed by a constant-rate clock



- A microprocessor consists of many circuits operating simultaneously, each of which
  - ▣ takes in inputs at time  $T_{input}$ ,
  - ▣ takes time  $T_{execute}$  to execute the logic, and
  - ▣ produces outputs at time  $T_{output}$

 
# Combinational Circuits

- Circuits we have seen were combinational
  - ▣ when inputs change, the outputs change after a while (time = logic delay thru circuit)
  - ▣ Example: adder



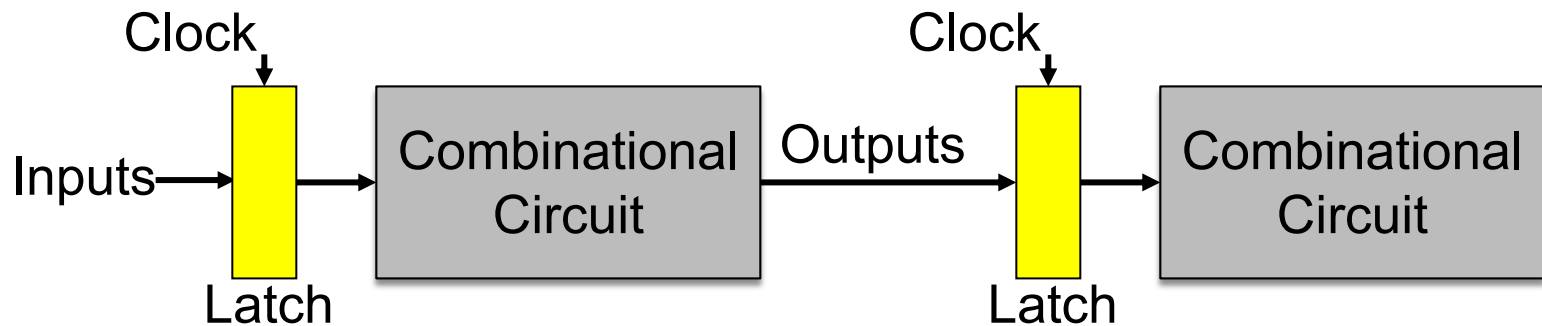
# Sequential Circuits

- Sequential circuit consists of combinational circuit and a storage element (latch)
- The clock acts like a start and stop signal
  - The latch ensures that the inputs to the circuit do not change during a clock cycle



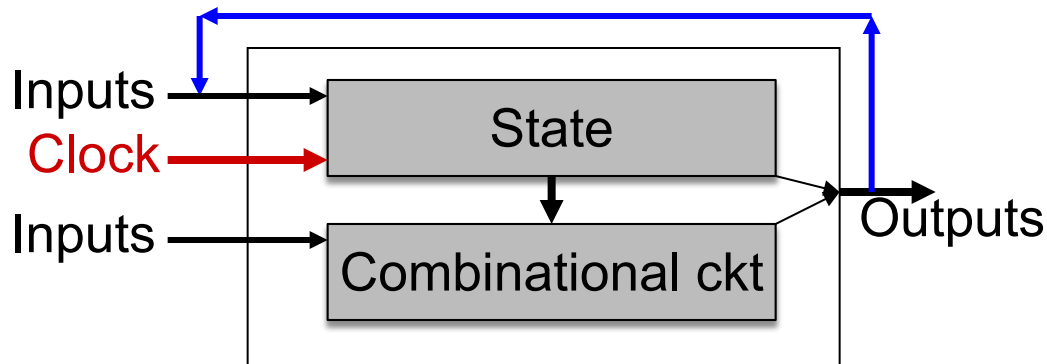
# Sequential Circuits

- At the start of the clock cycle, the rising edge causes the “state” storage to store some input values
- This state will not change for an entire cycle
- The combinational circuit has some time to accept the value of “state” and “inputs” and produce “outputs”
- Some of the outputs (for example, the value of next “state”) may feed back (but through the latch so they’re only seen in the next cycle)


 
# Design of an S-R Latch


- An S-R latch: set-reset latch
  - ▣ When Set is high, a 1 is stored
  - ▣ When Reset is high, a 0 is stored
  - ▣ When both are low, the previous state is preserved (hence, known as a storage or memory element)
  - ▣ Both are high – this set of inputs is not allowed




 
# Design of a D Latch

- The value of the input D signal (data) is stored only when the clock is high – the previous state is preserved when the clock is low



# Design of a D Flip Flop

- Latch vs. Flip Flop
  - ▣ Latch: outputs can change any time the clock is high (asserted)
  - ▣ Flip flop: outputs can change only on a clock edge
    - Technically, two D latches in series

